

3 SEM TDC PHYH (CBCS) C 7

2 0 2 2

(Nov/Dec)

PHYSICS

(Core)

Paper : C-7

(Digital Systems and Applications)

Full Marks : 53

Pass Marks : 21

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct answer (any *five*) : 1×5=5

(a) The shift of spot of light on the screen per unit change in voltage across the deflection plate is called

- (i) current sensitivity
- (ii) voltage sensitivity
- (iii) deflection sensitivity
- (iv) None of the above

(b) Linear ICs are used in

- (i) calculators
- (ii) computers
- (iii) TV and radio receivers
- (iv) counting circuits

- (c) The expression \overline{ABC} can be simplified to
- (i) $\overline{A} \cdot \overline{B} \cdot \overline{C}$
 - (ii) $AB + BC + CA$
 - (iii) $AB + \overline{C}$
 - (iv) $\overline{A} + \overline{B} + \overline{C}$
- (d) A half adder is constructed from
- (i) two XOR gates
 - (ii) one XOR gate and an OR gate with their inputs connected in parallel
 - (iii) one XOR gate and one AND gate with their inputs connected in parallel
 - (iv) one XOR gate and one NAND gate
- (e) A flip-flop is used to store
- (i) two bits of data
 - (ii) one bit of data
 - (iii) three bits of data
 - (iv) None of the above
- (f) Microprocessor 8085 has
- (i) 8-bit
 - (ii) 16-bit
 - (iii) 32-bit
 - (iv) None of the above

P23/58

(Continued)

2. Deduce an expression for deflection sensitivity of CRT. 3
- Or
- What is integrated circuit? How can transistor be fabricated in an IC? 3
3. Convert hexadecimal number 4 DFA into binary numbers. 2
4. Draw a circuit diagram for an AND gate using only NAND gates. 2
- Or
- How will you assemble an inverter by using NAND gate or NOR gate? 2
5. State and prove De Morgan's theorems. 3
6. What is Karnaugh map? Enter the following function on a Karnaugh map : 1+2=3
- $$F = ABC + \overline{A}BC + AB\overline{C}$$
- Or
- Prove the following expression, using laws of Boolean algebra : 3
- $$(AB + C)(AB + D) = AB + CD$$
7. Explain the circuit diagram of a full adder with truth table. 4
- Or
- What is the difference between adder and subtractor? Explain the circuit diagram of a half-subtractor. 1+3=4

P23/58

(Turn Over)

8. What is a flip-flop? What is its importance in digital system? Explain the operation of *J-K* flip-flop. 1+1+3=5
9. (a) What is multivibrator? Distinguish between astable and monostable multivibrators. 1+1=2
- (b) Draw the logic diagram of 4-bit parallel in-parallel out shift register. 2
10. What is a counter? What is the difference between decade counter and synchronous counter? 1+3=4
11. (a) Distinguish between volatile memory and non-volatile memory. Draw the block diagram of an 8×8 memory chip. How is information written in memory cell? 2+3+1=6
- (b) Define primary and secondary memories. 2
12. (a) Explain with necessary diagram, the functions of different pins of 8085 microprocessor. 5
- (b) What is data bus? Is it unidirectional? 1+1=2
- (c) Define assembler. What is the basic difference between arithmetic instruction and logical instruction? 1+2=3
